



East West University

Department of Computer Science and Engineering

Semester: Fall 2023

Course Number: CSE345

Section: 03

Course Title: Digital Logic Design

Group Number: 01

Project Number: Project-1

Group Members:

- i) 2021-2-60-063 (MD. Ismail Bhuiyan)
- ii) 2020-1-60-172 (Tanvir Ahmed)
- iii) 2020-2-60-123 (Rihan Mahmud)

Submitted To,

Musharrat Khan

Senior Lecturer

Department of Computer Science and Engineering

East West University

1. Problem Statement: A 4-bit code converter for odd parity converts the 4-bit input to 5-bit output so that odd parity is ensured.

2. Design Details:

Let's say 4-bit inputs are A3, A2, A1, A0 and 5-bit outputs are O3, O2, O1, O0, and P where, O3, O2, O1, O0 outputs are equivalent to the inputs A3, A2, A1, and A0 respectively and P is the parity bit.

Truth Table:

Input				Output				
A3	A2	A1	A0	O3	O2	O1	O0	P
0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	1	0
0	0	1	0	0	0	1	0	0
0	0	1	1	0	0	1	1	1
0	1	0	0	0	1	0	0	0
0	1	0	1	0	1	0	1	1
0	1	1	0	0	1	1	0	1
0	1	1	1	0	1	1	1	0
1	0	0	0	1	0	0	0	0
1	0	0	1	1	0	0	1	1
1	0	1	0	1	0	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	0	1	1	0	0	1
1	1	0	1	1	1	0	1	0
1	1	1	0	1	1	1	0	0
1	1	1	1	1	1	1	1	1

Here,

O3 = A3;

O2 = A2;

O1 = A1;


O0 = A0;

For Parity bit P, K-map:


$A_3 A_2 / A_1 A_0$	00	01	11	10
00	1		1	
01		1		1
11	1		1	
10		1		1

$$\therefore P = A_3'A_2'A_1'A_0' + A_3'A_2'A_1A_0 + A_3'A_2A_1'A_0 + A_3'A_2A_1A_0' + A_3A_2'A_1'A_0 + A_3A_2'A_1A_0' + A_3A_2A_1'A_0' + A_3A_2A_1A_0$$

3. Logic Diagram:

 


Simulation Results:

 

4. Structural Verilog Code:

```
module OddParity1(input A3,A2,A1,A0,output O3,O2,O1,O0,P);  
  
    wire w1,w2,w3,w4,w5,w6,w7,w8;  
  
    and g1(w1,~A3,~A2,~A1,~A0),  
        g2(w2,~A3,~A2,A1,A0),  
        g3(w3,~A3,A2,~A1,A0),  
        g4(w4,~A3,A2,A1,~A0),  
        g5(w5,A3,~A2,~A1,A0),  
        g6(w6,A3,~A2,A1,~A0),  
        g7(w7,A3,A2,~A1,~A0),  
        g8(w8,A3,A2,A1,A0);  
  
    or   g9(P,w1,w2,w3,w4,w5,w6,w7,w8),  
        g10(O0,A0),  
        g11(O1,A1),  
        g12(O2,A2),  
        g13(O3,A3);  
  
endmodule
```

Simulation Results:

 


5. Behavioral Verilog Code:

5.1. Procedural Model:

```
module OddParity2(input A3,A2,A1,A0, output reg O3,O2,O1,O0,P);  
    always@(A3,A2,A1,A0)  
        begin  
            O3=A3;  
            O2=A2;  
            O1=A1;  
            O0=A0;  
            P=0;  
            if(~A3&~A2&~A1&~A0) P=1;  
            if(~A3&~A2&A1&A0) P=1;  
            if(~A3&A2&~A1&A0) P=1;  
            if(~A3&A2&A1&~A0) P=1;  
            if(A3&~A2&~A1&A0) P=1;  
            if(A3&~A2&A1&~A0) P=1;  
            if(A3&A2&~A1&~A0) P=1;  
            if(A3&A2&A1&A0) P=1;  
        end  
endmodule
```

Simulation Results:

 

5.2. Continuous Assign Statement:

```
module OddParity3(input A3,A2,A1,A0, output O3,O2,O1,O0,P);
```

```
    assign O3=A3;
```

```
    assign O2=A2;
```

```
    assign O1=A1;
```

```
    assign O0=A0;
```

```
    assign P = (~A3&~A2&~A1&~A0) | (~A3&~A2&A1&A0) | (~A3&A2&~A1&A0) |  
              (~A3&A2&A1&~A0) | (A3&~A2&~A1&A0) | (A3&~A2&A1&~A0) |  
              (A3&A2&~A1&~A0) | (A3&A2&A1&A0);
```

```
endmodule
```

Simulation Results:

